
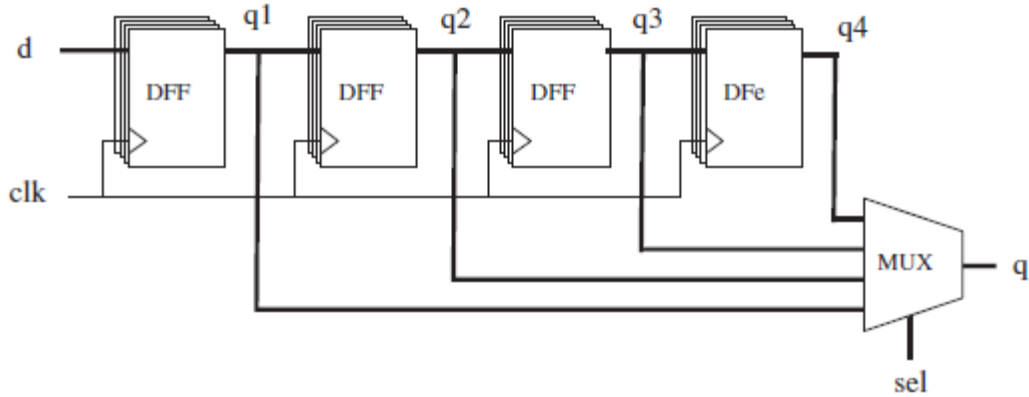


Q1) Figure below shows the diagram of a programmable data delay circuit. The input (d) and output (q) are 4-bit buses. Depending on the value of sel (select), q should be one, two, three, or four clock cycles delayed with respect to d.

 - (a) Write a VHDL code for this circuit;
- (b) How many flip-flops do you expect your solution to contain?
- (c) Synthesize your solution and open the report file. Verify whether the actual number of flip-flops matches your prediction.



Q2) For the D flip flop given in the figure below you are asked to examine each of the solutions below and determine whether q and qbar will work properly. Briefly explain your answers.



```

-----
ENTITY dff IS
PORT ( d, clk: IN BIT;
      q, qbar: BUFFER BIT);
END dff;

```

----- Solution 1 -----

```

ARCHITECTURE arch1 OF dff IS
    SIGNAL temp: BIT;
    BEGIN
        PROCESS (clk)
            BEGIN
                IF (clk'EVENT AND clk='1') THEN
                    temp <= d;
                    q <= temp;
                    qbar <= NOT temp;
                END IF;
            END PROCESS;
        END arch1;

```

----- Solution 2 -----

```
ARCHITECTURE arch2 OF dff IS
  SIGNAL temp: BIT;
  BEGIN
    PROCESS (clk)
      BEGIN
        IF (clk'EVENT AND clk='1') THEN
          temp <= d;
        END IF;
        q <= temp;
        qbar <= NOT temp;
      END PROCESS;
    END arch2;
```

----- Solution 3 -----

```
ARCHITECTURE arch3 OF dff IS
  SIGNAL temp: BIT;
  BEGIN
    PROCESS (clk)
      BEGIN
        IF (clk'EVENT AND clk='1') THEN
          temp <= d;
        END IF;
      END PROCESS;
    q <= temp;
    qbar <= NOT temp;
  END arch3;
```

-----

Q3) For the D flip flop in the previous question You are asked to examine each of the solutions below and determine whether q and qbar will work as expected. Briefly explain your answers.

```
-----
ENTITY dff IS
  PORT ( d, clk: IN BIT;
        q: BUFFER BIT;
        qbar: OUT BIT);
END dff;
```

----- Solution 1 -----

```
ARCHITECTURE arch1 OF dff IS
  BEGIN
    PROCESS (clk)
      VARIABLE temp: BIT;
      BEGIN
        IF (clk'EVENT AND clk='1') THEN
          temp := d;
          q <= temp;
        END IF;
      END PROCESS;
  END arch1;
```

```
                qbar <= NOT temp;
            END IF;
        END PROCESS;
    END arch1;
```

----- Solution 2 -----

```
ARCHITECTURE arch2 OF dff IS
BEGIN
    PROCESS (clk)
        VARIABLE temp: BIT;
        BEGIN
            IF (clk'EVENT AND clk='1') THEN
                temp := d;
                q <= temp;
                qbar <= NOT q;
            END IF;
        END PROCESS;
    END arch2;
```

----- Solution 3 -----

```
ARCHITECTURE arch3 OF dff IS
BEGIN
    PROCESS (clk)
        VARIABLE temp: BIT;
        BEGIN
            IF (clk'EVENT AND clk='1') THEN
                temp := d;
                q <= temp;
            END IF;
        END PROCESS;
    qbar <= NOT q;
    END arch3;
-----
```