

# Arithmetic Comparison Circuits

28.03.2011

$A, B$  are two unsigned binary numbers.

Comparator outputs

}	$A \text{ eq } B$	$(A = B)$
	$A \text{ gt } B$	$(A > B)$
	$A \text{ lt } B$	$(A < B)$

ex  $n = 4$

$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$

Intermediate signals:

$$\hat{c}_3 = \overline{a_3 \oplus b_3}$$

$$\hat{c}_2 = \overline{a_2 \oplus b_2}$$

$$\hat{c}_1 = \overline{a_1 \oplus b_1}$$

$$\hat{c}_0 = \overline{a_0 \oplus b_0}$$

$$\text{if } \hat{c}_3 \cdot \hat{c}_2 \cdot \hat{c}_1 \cdot \hat{c}_0 = 1$$

$$A = B$$

$A > B$

$$a_3 \bar{b}_3 + \overset{i_3}{i_3} a_2 \bar{b}_2 + \overset{i_3 \cdot i_2}{i_3 \cdot i_2} a_1 \bar{b}_1 + \overset{i_3 \cdot i_2 \cdot i_1}{i_3 \cdot i_2 \cdot i_1} a_0 \bar{b}_0 = A > B$$

check if the previous bits are equal.

$A = 1011$

$B = 0101$

$a_3 \cdot \bar{b}_3 = 1$

$A > B$

$$= a_3 \bar{b}_3 + i_3 \cdot a_2 \bar{b}_2 + i_3 \cdot i_2 \cdot a_1 \bar{b}_1 + i_3 \cdot i_2 \cdot i_1 \cdot a_0 \bar{b}_0$$




$A < B$ :

$$\bar{a}_3 b_3 + \bar{a}_3 \cdot \bar{a}_2 b_2 + \bar{a}_3 \cdot \bar{a}_2 \cdot \bar{a}_1 b_1 + \bar{a}_3 \cdot \bar{a}_2 \cdot \bar{a}_1 \cdot b_0$$

or  $A < B = \overline{A \text{ eq } B + A > B}$

making a 2's complement subtraction ( $X - Y$ ):

example :

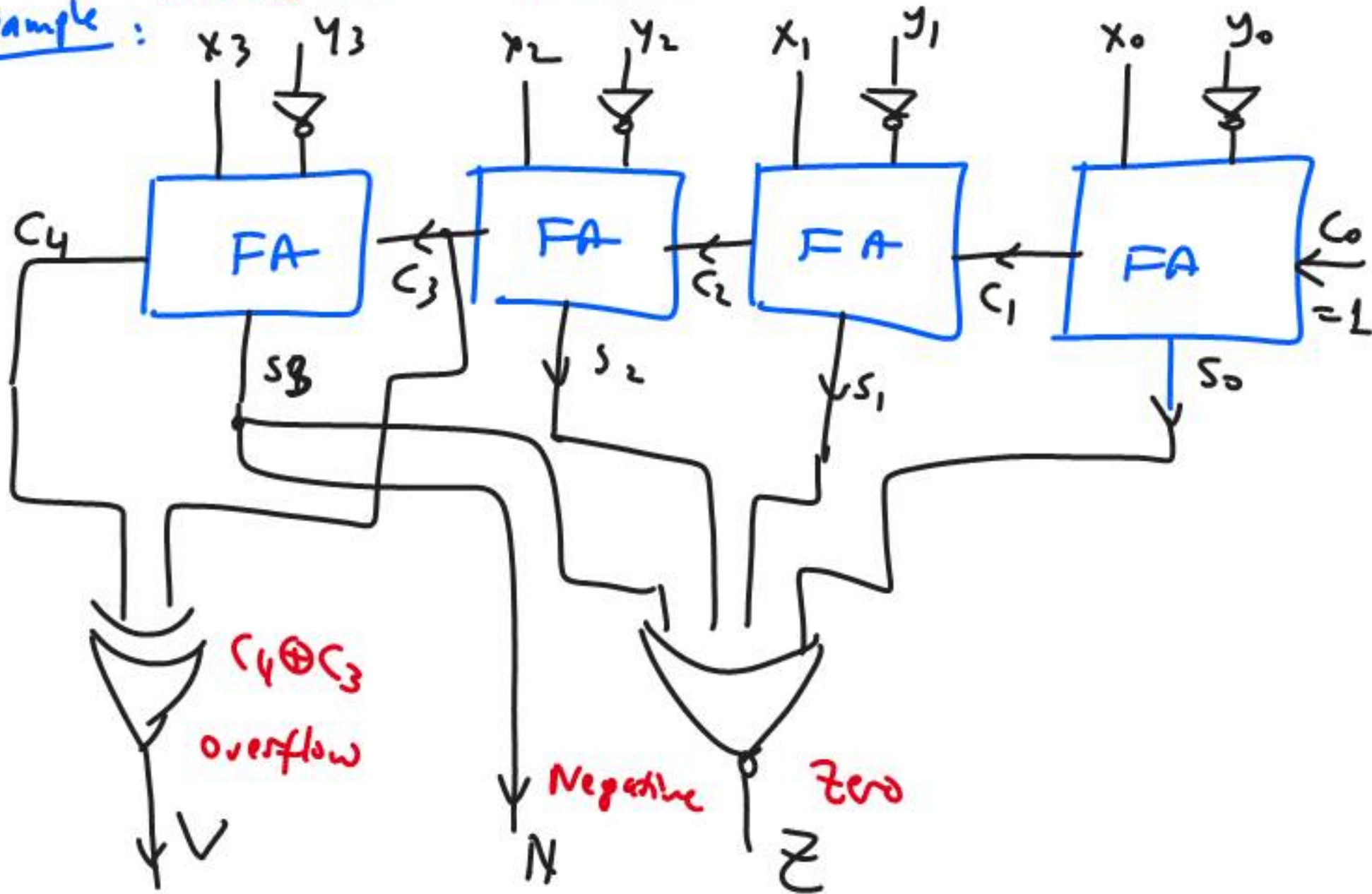

## STRUCTURAL VHDL CODE:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
USE work.fulladd_package.all;
```

```
ENTITY COMPARATOR IS
```

```
PORT ( X, Y : IN STD_LOGIC_VECTOR ( 3 DOWN TO 0 );
```

```
      V, N, Z : OUT STD_LOGIC );
```

```
END COMPARATOR;
```

ARCHITECTURE Structure OF COMPARATOR U

```
SIGNAL S : STD_LOGIC_VECTOR ( 3 DOWN TO 0 );
```

```
SIGNAL C : STD_LOGIC_VECTOR ( 1 TO 4 );
```



BEGIN

Stage 0: full add PORTMAP ('1', X(0), NOT Y(0), S(0), C(1));

Stage 1: " " " (C(1), X(1), NOT Y(1), S(1), C(2));

Stage 2: " " " (C(2), X(2), NOT Y(2), S(2), C(3));

Stage 3: " " " (C(3), X(3), NOT Y(3), S(3), C(4));

Co is always '1'

V ← C(4) XOR C(3);

Z ← '1' WHEN S(3 DOWN TO 0) = "0000";

N ← S(3);

END STRUCTURE;

① If  $x < y \Rightarrow$   $x - y$  operation we are doing

a)  $x$  and  $y$  are of the same sign

$$\begin{array}{r} x \\ - y \\ \hline \end{array} \Rightarrow \begin{array}{r} x \\ + -y \\ \hline \end{array}$$

$V = 0$   
 $N = 1$

No overflow

① result is always negative ✓

b)  $x$  and  $y$  are of the opposite signs.

$x = -5$   
 $y = +4$

$-5 - (+4) = -9$

$x$  is negative  $x - y =$

$y$  is positive  $-2 \quad 3 \quad -2 - (3) = -5$

$$\begin{array}{r} 0101 \quad 0100 \\ 1010 \quad 1000 \\ \hline 1011 \quad 1101 \\ \hline \phantom{1011} \quad -5 \end{array}$$

$x$  is positive  
 $x$  is negative

~~$x < y$~~

$N = 1$   
 $V = 0$

② If there is no overflow.

$$\begin{array}{r} 1011 \\ +1001 \\ \hline 10100 \end{array}$$

→ here is overflow  $V = 1$   
 $N = 0$  ③

$\therefore$  we can write  $N \oplus V = L$  for  $X < Y$ . in  $X - Y$ .

$$* X = Y \Rightarrow z = 1$$

$$* X \leq Y \Rightarrow z + N \oplus V = L$$

$$* X > Y = \overline{(X \leq Y)} \Rightarrow \overline{(z + N \oplus V)} = 1$$

$$* X \geq Y = z + \overline{(z + N \oplus V)} = 1 \quad \left| \begin{array}{l} = \overline{X < Y} \\ = \overline{N \oplus V} = 1 \end{array} \right.$$
$$z + \bar{z} \cdot \overline{(N \oplus V)} = 1$$
$$\underbrace{(z + \bar{z})}_1 \cdot \overline{(z + N \oplus V)} = 1$$