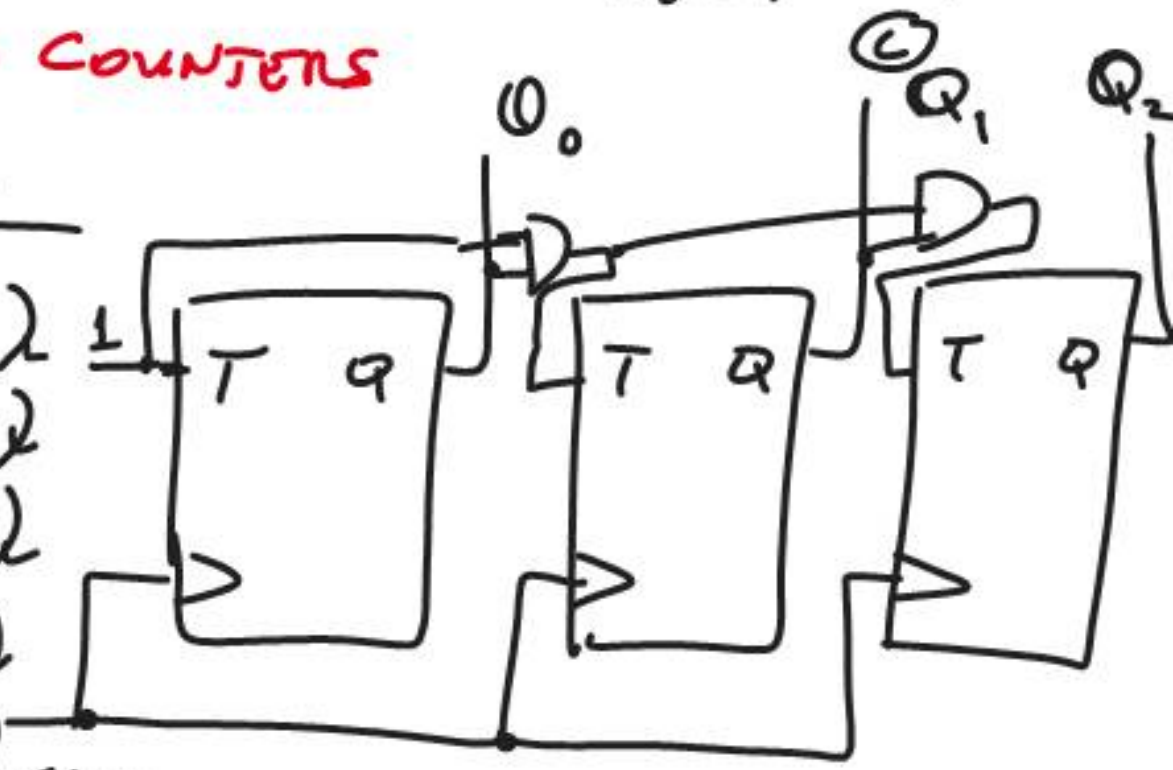


18.04.2011

SYNCHRONOUS COUNTERS

Clock Cycle	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0





$$T_0 = 1$$

$$T_1 = Q_0 \cdot 1$$

$$T_2 = Q_1 \cdot Q_0 \cdot 1$$

synchronous binary up-counter

Synchronous up-counter with D-FFs

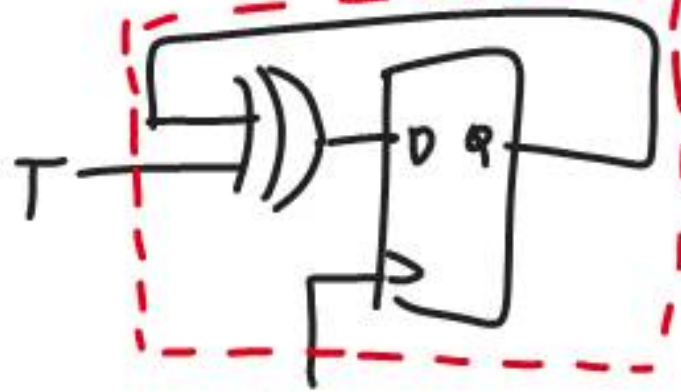 

fanout:
of gates a
gate can
drive.

4-bit binary
counter
with 0 FFs.

$$D_0 = Q_0 \oplus \text{Enable}$$


$$D_1 = Q_1 \oplus Q_0 \cdot \text{Enable}$$

$$D_2 = Q_2 \oplus Q_1 Q_0 \cdot \text{Enable}$$

$$D_3 = Q_3 \oplus Q_2 Q_1 Q_0 \dots$$

Normally in a Finite State Machine (FSM, a counter is an FSM)
The FF inputs for the next states are calculated.

Ex:

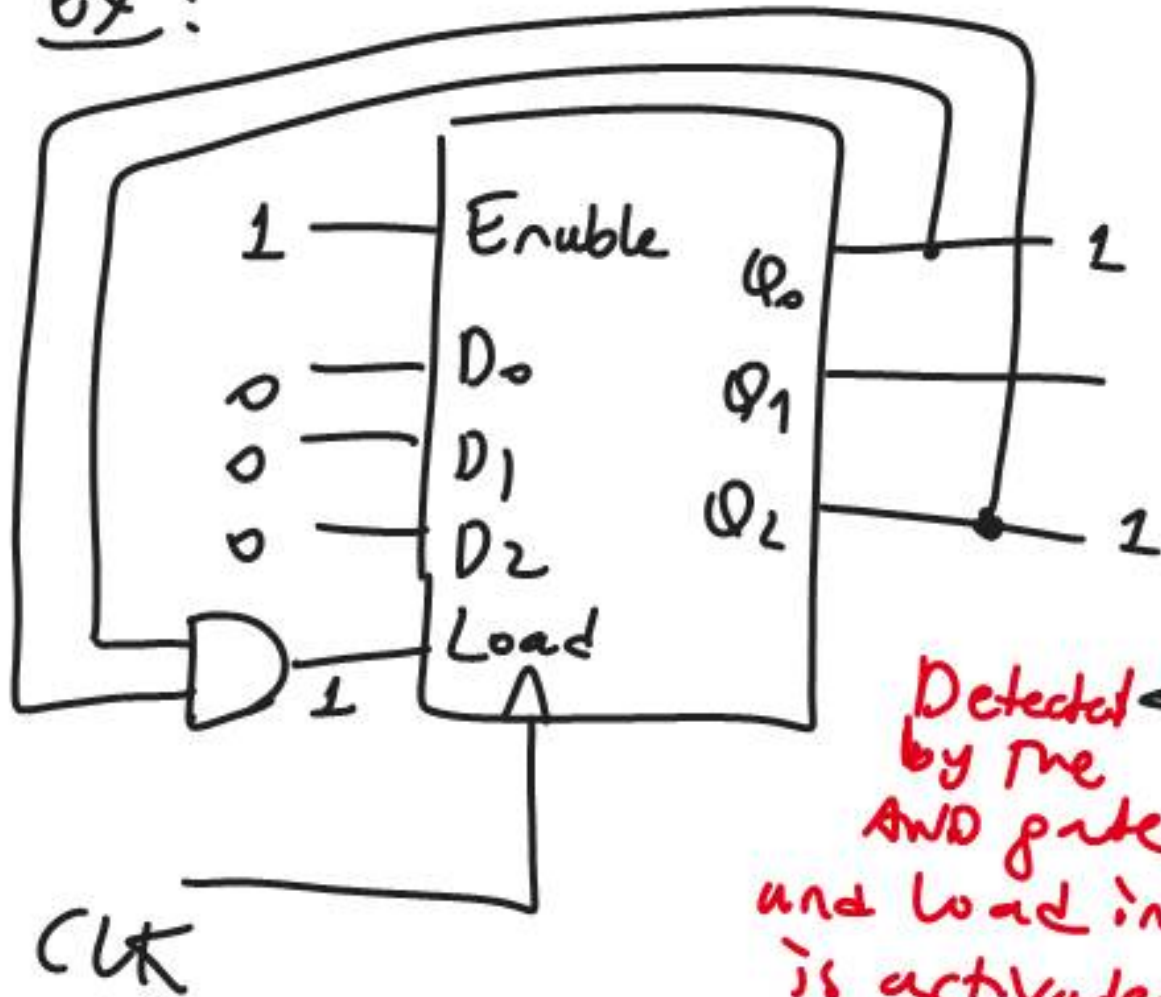


A modulo 6 counter:

Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
0	0	0


Detected by the AND gate and load input is activated

This is loaded into the D FFs

 

Inside of the previous modulo-6 counter




ex: A BCD counter (2 digits)

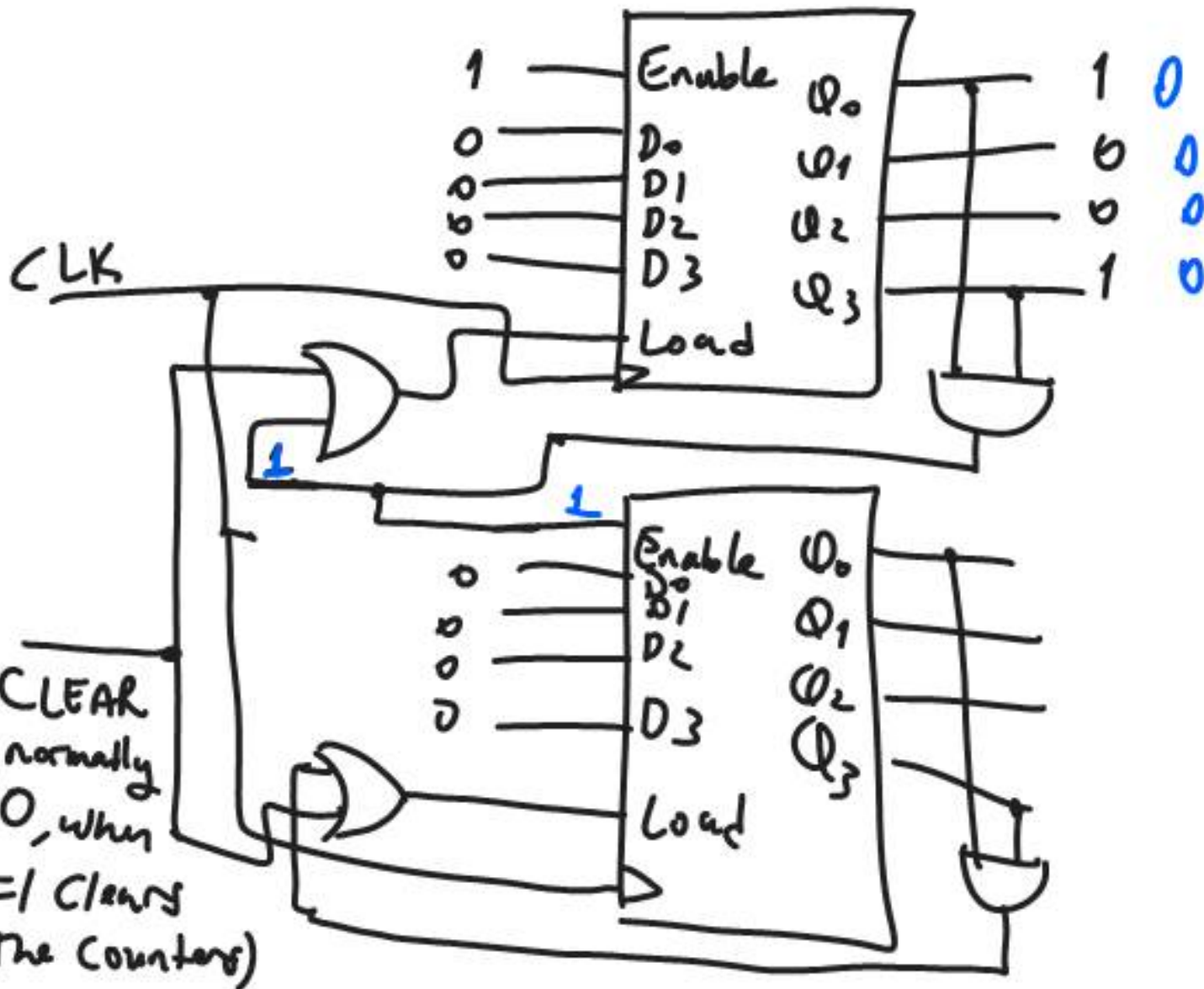

B ₁₀	B ₂	DECIMAL
0	0	
0	0	0
0	1	1
0	0	2
0	1	3
0	0	4
0	1	5
0	0	6
0	1	7
0	0	8
0	1	9
1	0	10
1	0	11
1	1	12
1	0	13
1	1	14
1	0	15

CLEAR normally 0, when = 1 clears the counters)

A RING COUNTER

  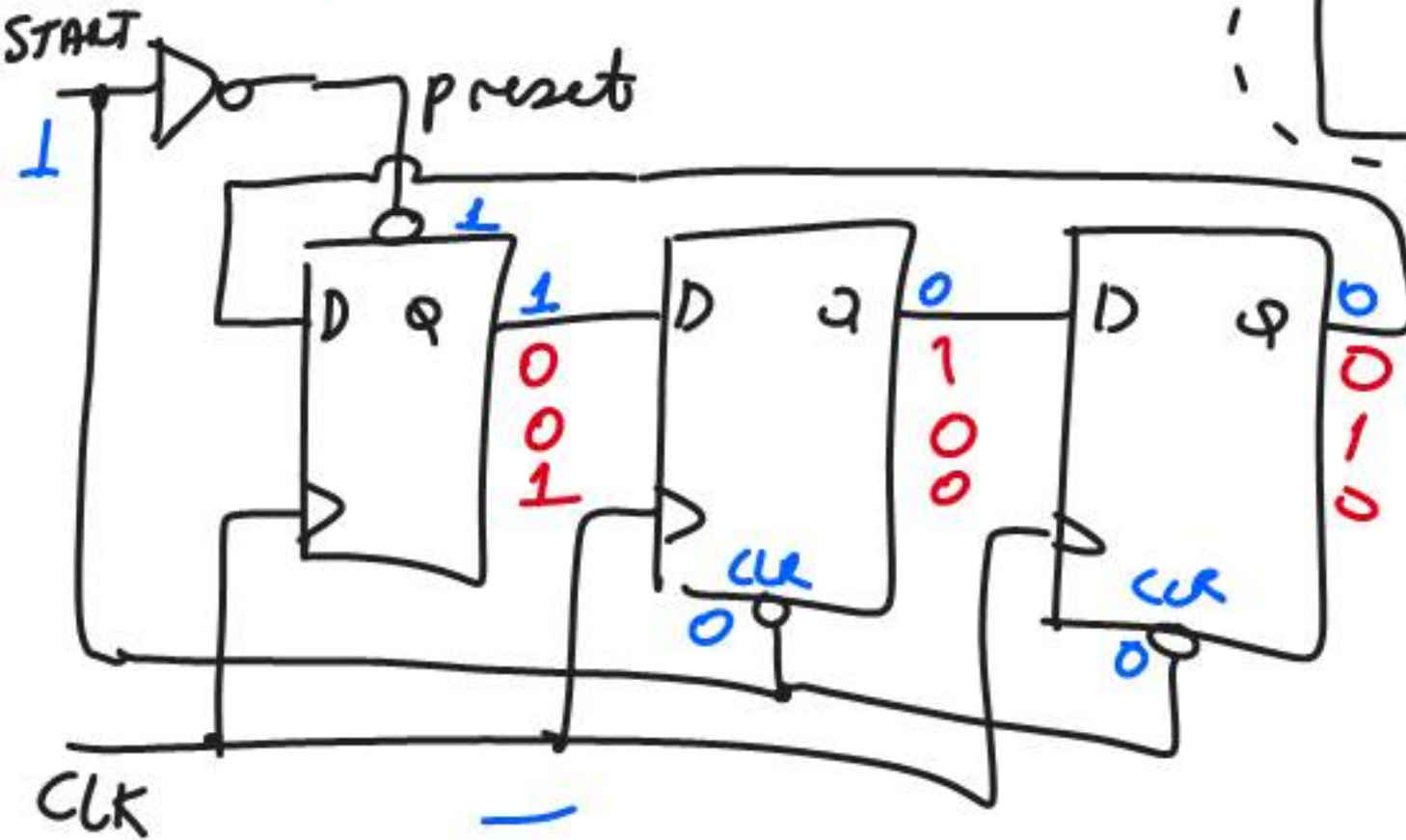

7 will rotate

A Four-bit Ring Counter

