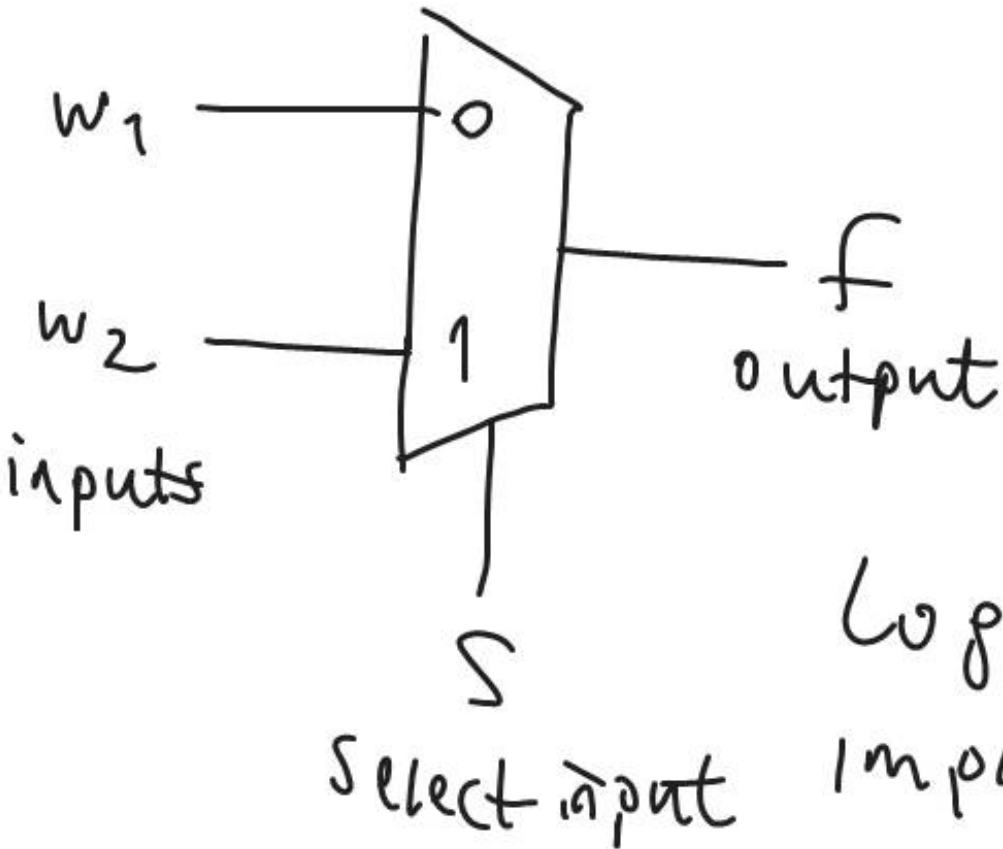


# A MULTIPLEXER

477  
17.02.2011

©

A 2-to-1 mux



$s$	$f$
0	$w_1$
1	$w_2$


$$f(w_1, w_2) = \bar{S} w_1 + S w_2$$

Logic functions can be implemented by multiplexers.

Shannon's Theorem.

$$f(S, w_1, w_2) = \bar{S}w_1 + Sw_2$$


STRUCTURAL  
way of representing  
mux

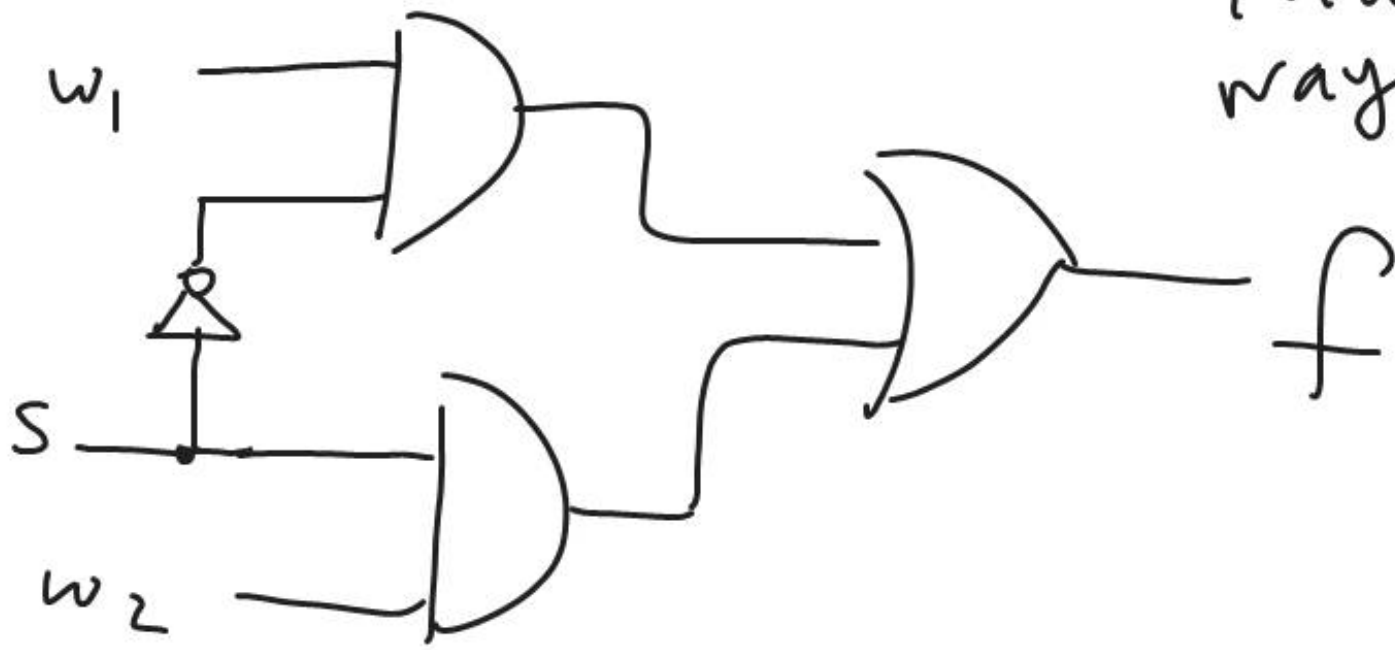

a BEHAVIORAL  
way of representing  
the mux

VHDL code for the mux:

STRUCTURAL

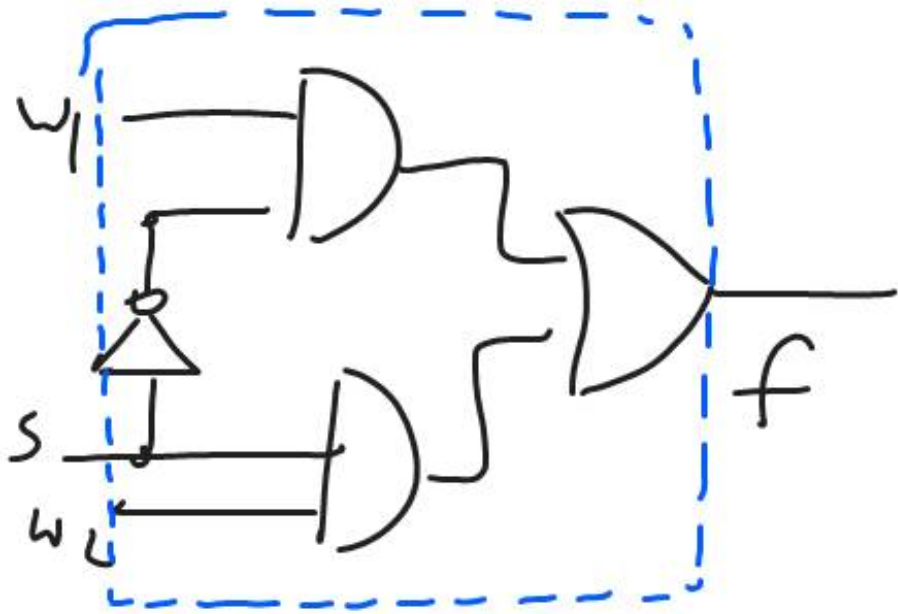


INPUTS

w1  
w2  
s

OUTPUT(S)

f

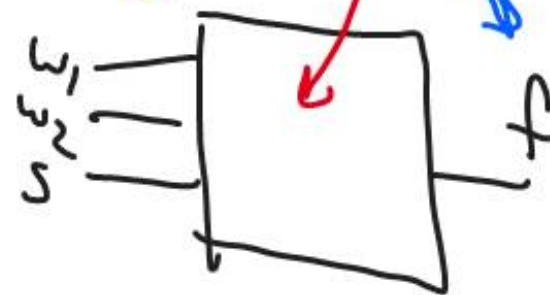

VHDL

```

ENTITY mux2to1 IS
PORT (w1, w2, s : IN BIT;
      f : OUT BIT);
END mux2to1;

```

ARCHITECTURE Structure of


```

mux2to1 IS
BEGIN
f <= (w1 AND NOT s) OR (
w2 AND s);
END Structure;

```

# BEHAVIORAL

# VHDL CODE OF mux

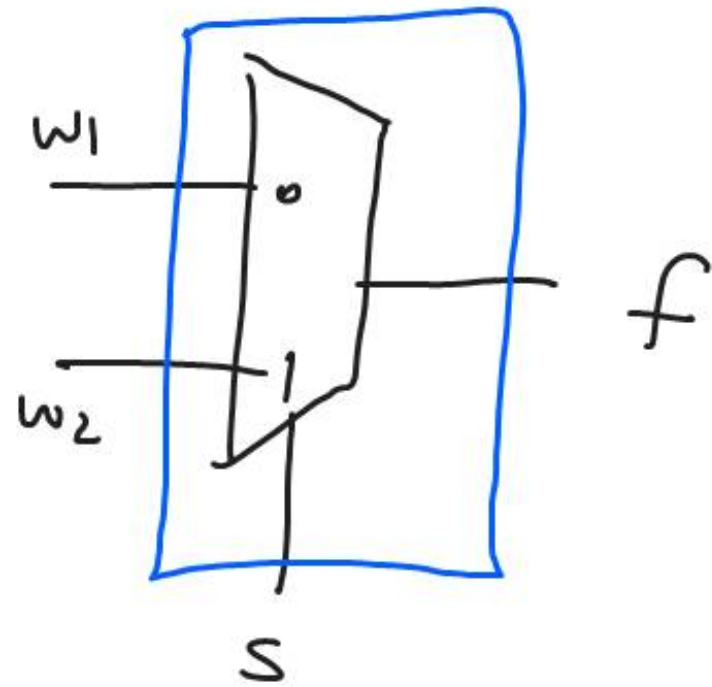

ENTITY mux2to1 IS

```
PORT (w1, w2, s : IN BIT;  
      f : OUT BIT);
```

```
END mux2to1;
```

ARCHITECTURE Behavior of mux2to1

```
BEGIN
```

with S SELECT


```
f <= w1 when '0'
```

```
w2 when OTHERS;
```

```
END Behavior;
```

3

If we have a 4-to-1 mux:  
BEHAVIOR:

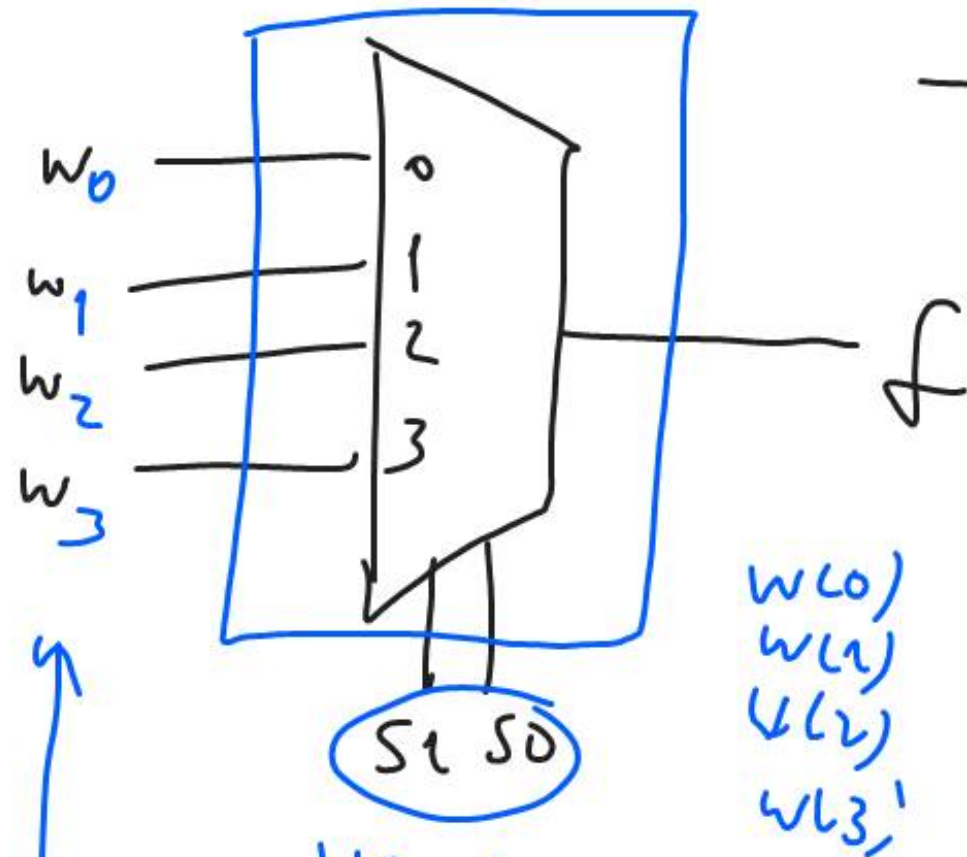

Vector  
 00  
 01  
 10  
 11  
 ⋮

wires

```
ENTITY mux4to1 IS
  PORT ( W = IN STD_LOGIC
        VECTOR (0 TO 3);
        S : IN STD_LOGIC_VECTOR
              (1 DOWN TO 0);
        f : OUT STD_LOGIC );
END mux4to1;
```

ARCHITECTURE Behavior of Mux4to1 IS  
 BEGIN  
 ↓

WITH S SELECT

$f \leftarrow w(0)$  WHEN "00";

$w(1)$  WHEN "01";

$w(2)$  WHEN "10";

$w(3)$  WHEN OTHERS;

END Behavior;


'0', '1'

"00"

"01001"


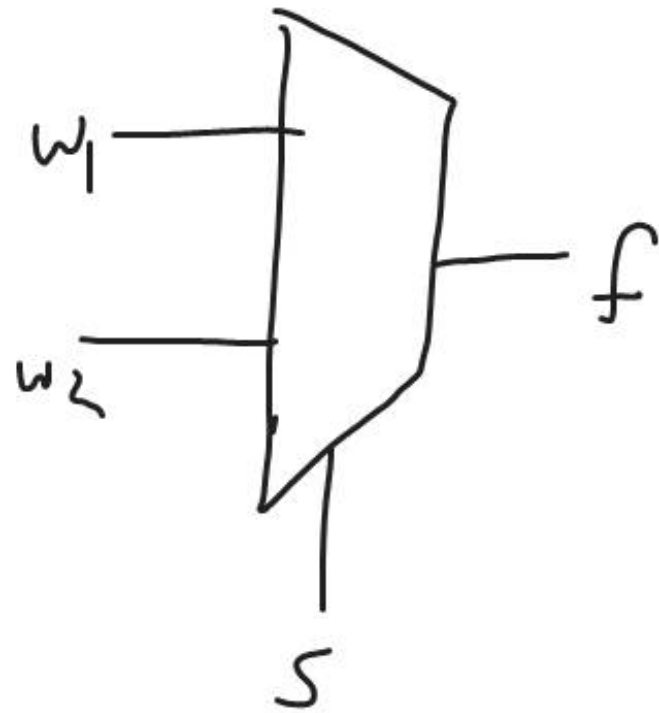
$$f(s, w_1, w_2) = m(2) + m(3) + m(5) + m(7)$$



minterms

Sum of Products (SOP)

s	w <sub>1</sub>	w <sub>2</sub>	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$m(0)$

$m(1)$

$m(2)$


$m(3)$

$m(4)$

$m(5)$

$m(6)$

$m(7)$

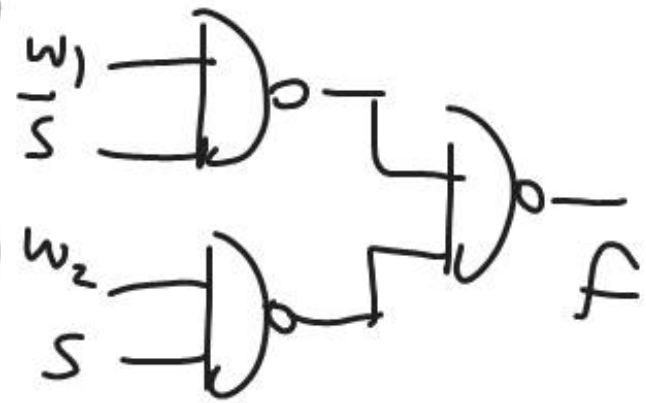

Truth Table:

s	w <sub>1</sub>	w <sub>2</sub>	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$f = \bar{s}w_1 + sw_2$$


ex 3

# Implementing with MUXs (Shannon's Theorem)

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3 \quad \text{Majority function}$$

$$f(w_1, w_2, w_3) = \bar{w}_1 f(\bar{w}_1) + w_1 f(w_1)$$

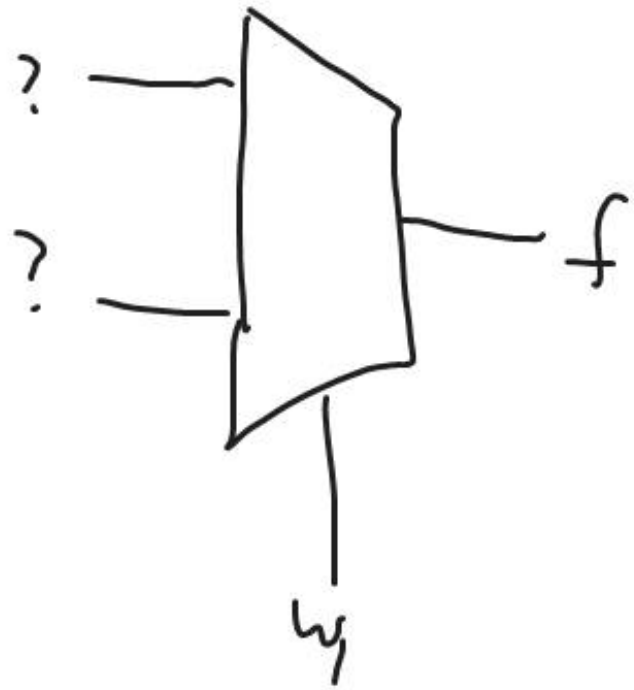$\downarrow$  cofactors of  $\bar{w}_1$       cofactors of  $w_1$



$$\begin{aligned}
 f &= w_1 w_2 + w_1 w_3 + w_2 w_3 \quad \underbrace{1}_{(\bar{w}_1 + w_1)} \\
 &= w_1 (w_2 + w_3) + w_2 w_3 (\bar{w}_1 + w_1) \\
 &= w_1 (w_2 + w_3) + \bar{w}_1 w_2 w_3 + w_2 w_3 w_1 \\
 &= w_1 (w_2 + w_3) + w_1 w_2 w_3 + \bar{w}_1 w_2 w_3
 \end{aligned}$$



$$= \bar{w}_1 w_2 w_3 + w_1 (w_2 + w_3) + w_1 w_2 w_3$$


$$= \bar{w}_1 w_2 w_3 + w_1 \underbrace{\left[ w_2 + w_3 + w_2 w_3 \right]}_{w_2 + w_3 (1 + w_2)}$$


$f(\bar{w}_1)$

$f(w_1)$

$$w_2 + w_3 \cdot 1 = w_2 + w_3$$
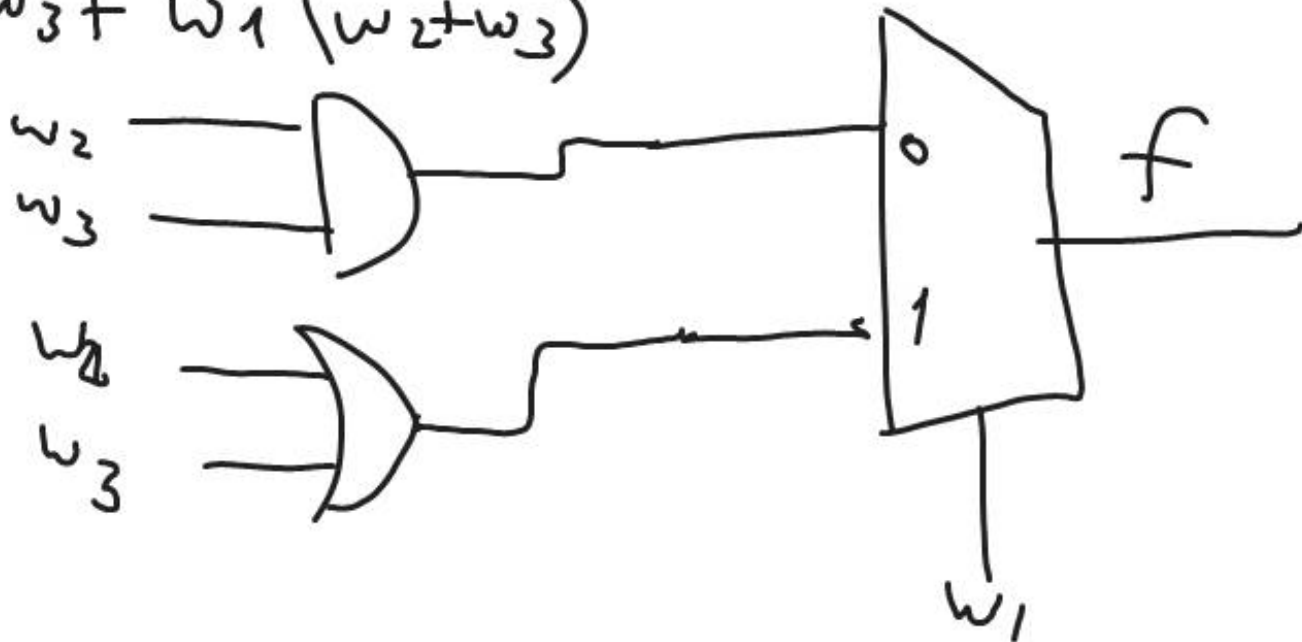
$$f = \bar{w}_1 w_2 w_3 + w_1 (w_2 + w_3)$$



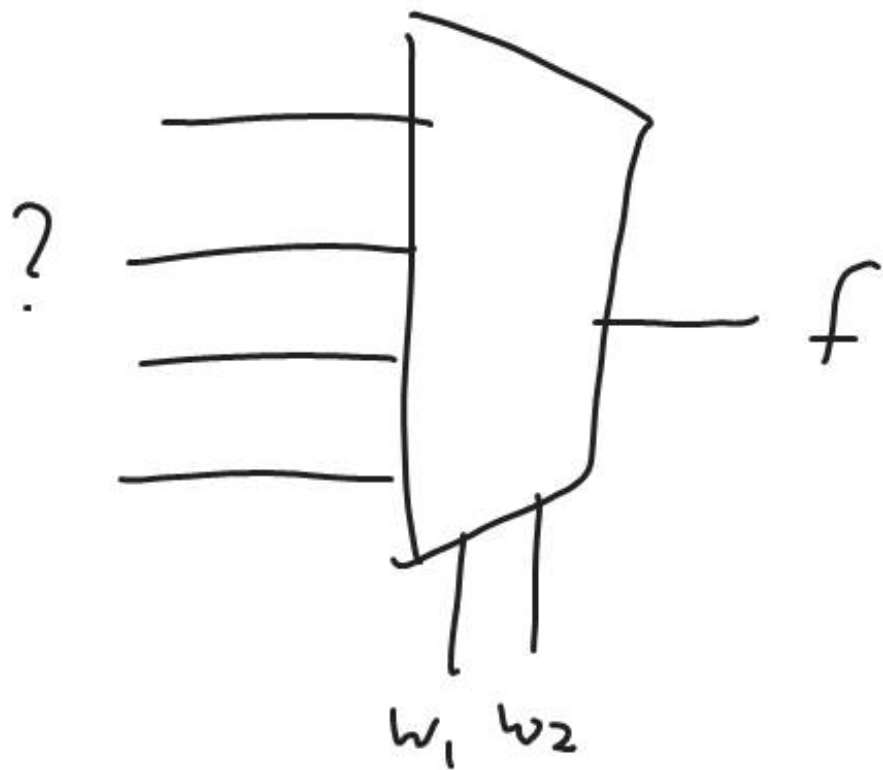

$$f = \bar{w}_1 \bar{w}_2 (\text{?}) + \bar{w}_1 w_2 ( ) + w_1 \bar{w}_2 ( ) + w_1 w_2 ( )$$

# DESIGN OF DIGITAL ICs

Design

