

ECE 477 LAB 11

- 1) By using the solution of Q3 in lab work 10 upload the modified counter implementation to the Genesys board.
- 2) Modify the question 1 to 0-255 counter. Do related simulations.
- 3) Define an input that controls the counter whether counts up or down. Modify the question 2.
- 4) A new type of clock divider will be introduced.

Homework

- 1) 2's complements circuit
- 2) 8-Bit Magnitude Comparator
- 3) 16-Bit Magnitude Comparator
- 4) 32-Bit Magnitude Comparator
- 5) 1's complements circuit (by using XOR gates)