

ECE 477 LAB 4

- 1) Matrix calculation in VHDL will be explained during the lab session. Download and open the sample project form the “<http://ece477.cankaya.edu.tr/course.php?page=12>”.

$$\begin{bmatrix} 2 & 1 \end{bmatrix} * \begin{bmatrix} 2 & 3 \\ 4 & 5 \end{bmatrix} = \begin{bmatrix} 8 & 8 \end{bmatrix}$$

- 2) Complete the example code in order to get full matrix multiplication result.
- 3) Modify the example code 1x3 array * 3x3 array form and do the related simulations.

$$\begin{bmatrix} 1 & 2 & 3 \end{bmatrix} * \begin{bmatrix} 3 & 0 & 1 \\ 7 & 2 & 9 \\ 1 & 2 & 1 \end{bmatrix} = \begin{bmatrix} 20 & 10 & 22 \end{bmatrix}$$

Homework

- 1) Design an 2^N -to-N Encoder with Enable. (Use “generic”)
- 2) Design a 16-to-4 Encoder with Enable. (Use “case”)
- 3) Design a 8-to-3 Encoder with Enable. (Use “when-else”)
- 4) Design a 4-to-2 Encoder with Enable. (Use “with-select”)
- 5) Design a 4-to-2 Encoder with Enable. (Use logic gates)