 


## Packages and Components

Frequently used pieces of code can be written in the form of COMPONENTS, FUNCTIONS, or PROCEDURES, then placed in a PACKAGE, which is finally compiled into the destination LIBRARY.



## PACKAGE

Frequently used pieces of VHDL code are usually written in the form of COMPONENTS, FUNCTIONS, or PROCEDURES.

Such codes are then placed inside a PACKAGE and compiled into the destination LIBRARY. The importance of this technique is that it allows code partitioning, code sharing, and code reuse.

Package syntax is presented below.

```
PACKAGE package_name IS
```

```
    (declarations)
```

```
END package_name;
```

```
[PACKAGE BODY package_name IS
```

```
    (FUNCTION and PROCEDURE descriptions)
```

```
END package_name;]
```

The syntax is composed of two parts: **PACKAGE** and **PACKAGE BODY**.

The first part is mandatory and contains all declarations, while the second part is necessary only when one or more subprograms (**FUNCTION** or **PROCEDURE**) are declared in the upper part, in which case it must contain the descriptions (bodies) of the subprograms. **PACKAGE** and **PACKAGE BODY** must have the same name.

The declarations list can contain the following: **COMPONENT**, **FUNCTION**, **PROCEDURE**, **TYPE**, **CONSTANT**, etc.

### **Example:** Simple Package

The example below shows a **PACKAGE** called `my_package`. It contains only **TYPE** and **CONSTANT** declarations, so a **PACKAGE BODY** is not necessary.

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 PACKAGE my_package IS
6     TYPE state IS (st1, st2, st3, st4);
7     TYPE color IS (red, green, blue);
8     CONSTANT vec: STD_LOGIC_VECTOR(7 DOWNTO 0) := "11111111";
9 END my_package;
10 -----

```

**Example:** Package with a Function

This example contains, besides TYPE and CONSTANT declarations, a FUNCTION.

Therefore, a PACKAGE BODY is now needed. This function returns TRUE when a positive edge occurs on clk.

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 PACKAGE my_package IS
6     TYPE state IS (st1, st2, st3, st4);
7     TYPE color IS (red, green, blue);
8     CONSTANT vec: STD_LOGIC_VECTOR(7 DOWNTO 0) := "11111111";
9     FUNCTION positive_edge(SIGNAL s: STD_LOGIC) RETURN BOOLEAN;

```

```

10 END my_package;
11 -----
12 PACKAGE BODY my_package IS
13     FUNCTION positive_edge(SIGNAL s: STD_LOGIC) RETURN BOOLEAN IS
14     BEGIN
15         RETURN (s'EVENT AND s='1');
16     END positive_edge;
17 END my_package;
18 -----

```

Any of the PACKAGES above can now be compiled, becoming then part of our work LIBRARY (or any other).

To make use of it in a VHDL code, we have to add a new USE clause to the main code (USE work.my\_package.all), as shown below.

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE work.my_package.all;
-----
ENTITY...
    ...
ARCHITECTURE...
    ...
-----

```

## **COMPONENT**

A COMPONENT is a way of partitioning a code and providing code sharing and code reuse.

For example, commonly used circuits, like flip-flops, multiplexers, adders, basic gates, etc., can be placed in a LIBRARY, so any project can make use of them without having to explicitly rewrite such codes.

### **COMPONENT declaration:**

```
COMPONENT component_name IS
    PORT (
        port_name : signal_mode signal_type;
        port_name : signal_mode signal_type;
        ...);
END COMPONENT;
```

### **COMPONENT instantiation:**

```
label: component_name PORT MAP (port_list);
```

**Example:** Inverter as a component

----- COMPONENT declaration: -----

```
COMPONENT inverter IS
```


```
    PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
```

```
END COMPONENT;
```


----- COMPONENT instantiation: -----

```
U1: inverter PORT MAP (x, y);
```

### Basic ways of declaring COMPONENTS

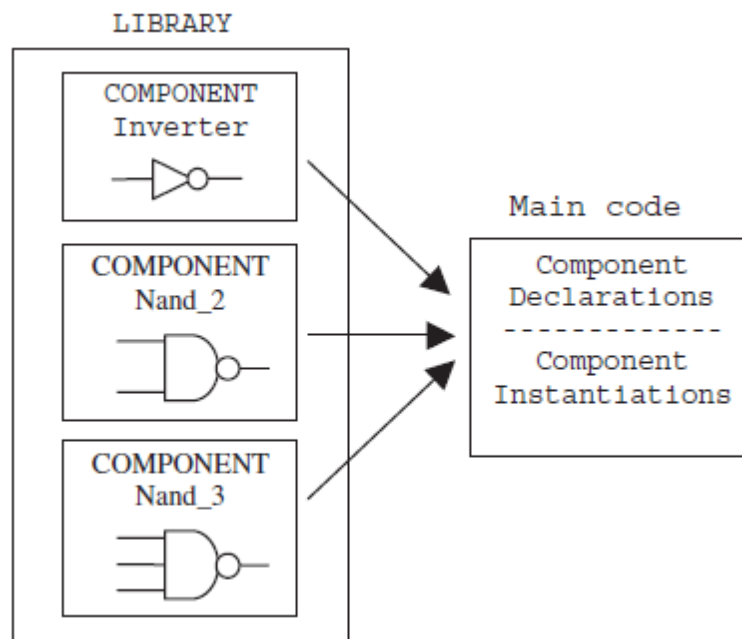


Declarations in the main code itself

 

Declarations in a PACKAGE.

 **Example:** Components Declared in the Main Code

Implement the circuit below employing only COMPONENTS (inverter, nand\_2, and nand\_3), but without creating a specific PACKAGE to declare them.



```

1 ----- File inverter.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY inverter IS
6     PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
7 END inverter;
8 -----
9 ARCHITECTURE inverter OF inverter IS
10 BEGIN
11     b <= NOT a;
12 END inverter;
13 -----

```

```

1 ----- File nand_2.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY nand_2 IS
6     PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
7 END nand_2;
8 -----
9 ARCHITECTURE nand_2 OF nand_2 IS
10 BEGIN
11     c <= NOT (a AND b);
12 END nand_2;

```



```

1 ----- File nand_3.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY nand_3 IS
6     PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
7 END nand_3;
8 -----
9 ARCHITECTURE nand_3 OF nand_3 IS
10 BEGIN
11     d <= NOT (a AND b AND c);
12 END nand_3;
13 -----

```

```

1 ----- File project.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY project IS
6     PORT (a, b, c, d: IN STD_LOGIC;
7           x, y: OUT STD_LOGIC);
8 END project;

```

```

10 ARCHITECTURE structural OF project IS
11 -----
12 COMPONENT inverter IS
13   PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
14 END COMPONENT;
15 -----
16 COMPONENT nand_2 IS
17   PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
18 END COMPONENT;
19 -----
20 COMPONENT nand_3 IS
21   PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
22 END COMPONENT;
23 -----
24 SIGNAL w: STD_LOGIC;
25 BEGIN
26   U1: inverter PORT MAP (b, w);
27   U2: nand_2 PORT MAP (a, b, x);
28   U3: nand_3 PORT MAP (w, c, d, y);
29 END structural;
30 -----
9 -----

```

### **Example:** Components Declared in a Package

We want to implement the same project of the previous example. However, we will now create a PACKAGE where all the COMPONENTS (inverter, nand\_2, and nand\_3) will be declared,

```
1 ----- File inverter.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY inverter IS
6     PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
7 END inverter;
8 -----
9 ARCHITECTURE inverter OF inverter IS
10 BEGIN
11     b <= NOT a;
12 END inverter;
13 -----

1 ----- File nand_2.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY nand_2 IS
6     PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
7 END nand_2;
8 -----
```

9 ARCHITECTURE nand\_2 OF nand\_2 IS

10 BEGIN

11 c <= NOT (a AND b);

12 END nand\_2;

13 -----

1 ----- File nand\_3.vhd: -----

2 LIBRARY ieee;

3 USE ieee.std\_logic\_1164.all;

4 -----

5 ENTITY nand\_3 IS

6 PORT (a, b, c: IN STD\_LOGIC; d: OUT STD\_LOGIC);

7 END nand\_3;

8 -----

9 ARCHITECTURE nand\_3 OF nand\_3 IS

10 BEGIN

11 d <= NOT (a AND b AND c);

12 END nand\_3;

13 -----

```

1 ----- File my_components.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 PACKAGE my_components IS
6 ----- inverter: -----
7 COMPONENT inverter IS
8     PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
9 END COMPONENT;
10 ----- 2-input nand: ---
11 COMPONENT nand_2 IS
12     PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
13 END COMPONENT;
14 ----- 3-input nand: ---
15 COMPONENT nand_3 IS
16     PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
17 END COMPONENT;
18 -----
19 END my_components;
20 -----

```

```

1 ----- File project.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 USE work.my_components.all;
5 -----
6 ENTITY project IS
7     PORT ( a, b, c, d: IN STD_LOGIC;
8           x, y: OUT STD_LOGIC);
9 END project;
10 -----
11 ARCHITECTURE structural OF project IS
12     SIGNAL w: STD_LOGIC;
13 BEGIN
14     U1: inverter PORT MAP (b, w);
15     U2: nand_2 PORT MAP (a, b, x);
16     U3: nand_3 PORT MAP (w, c, d, y);
17 END structural;
18 -----

```

## **PORT MAP**

There are two ways to map the PORTS of a COMPONENT during its instantiation: positional mapping and nominal mapping.

```
COMPONENT inverter IS
    PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
END COMPONENT;

...

U1: inverter PORT MAP (x, y);
```

In it, the mapping is positional; that is, PORTS x and y correspond to a and b, respectively. On the other hand, a nominal mapping would be the following:

```
U1: inverter PORT MAP (x=>a, y=>b);
```

Positional mapping is easier to write, but nominal mapping is less error-prone. Ports can also be left unconnected (using the keyword OPEN).

For example:


```
U2: my_circuit PORT MAP (x=>a, y=>b, w=>OPEN, z=>d);
```

## **GENERIC MAP**

GENERIC units can also be instantiated. In that case, a GENERIC MAP must be used in the COMPONENT instantiation to pass information to the GENERIC parameters.

```
label: compon_name GENERIC MAP (param. list) PORT MAP (port list);
```
 
### Example: Instantiating a Generic Component



```
1 ----- File parity_gen.vhd (component): -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY parity_gen IS
6     GENERIC (n : INTEGER := 7); -- default is 7
7     PORT ( input: IN BIT_VECTOR (n DOWNTO 0);
8           output: OUT BIT_VECTOR (n+1 DOWNTO 0));
9 END parity_gen;
10 -----
11 ARCHITECTURE parity OF parity_gen IS
12 BEGIN
13     PROCESS (input)
14         VARIABLE temp1: BIT;
15         VARIABLE temp2: BIT_VECTOR (output'RANGE);
16     BEGIN
17         temp1 := '0';
18         FOR i IN input'RANGE LOOP
19             temp1 := temp1 XOR input(i);
20             temp2(i) := input(i);
21         END LOOP;
```



22           temp2(output'HIGH) := temp1;

23           output <= temp2;

24 END PROCESS;

25 END parity;

26 -----

1 ----- File my\_code.vhd (actual project): -----

2 LIBRARY ieee;

3 USE ieee.std\_logic\_1164.all;

4 -----

5 ENTITY my\_code IS

6 GENERIC (n : POSITIVE := 2); -- 2 will overwrite 7

7           PORT ( inp: IN BIT\_VECTOR (n DOWNT0 0);

8                    outp: OUT BIT\_VECTOR (n+1 DOWNT0 0));

9 END my\_code;

10 -----

11 ARCHITECTURE my\_arch OF my\_code IS

12 -----

13 COMPONENT parity\_gen IS

14   GENERIC (n : POSITIVE);

15   PORT (input: IN BIT\_VECTOR (n DOWNT0 0);

16           output: OUT BIT\_VECTOR (n+1 DOWNT0 0));

17 END COMPONENT;

18 -----


19 BEGIN

20 C1: parity\_gen GENERIC MAP(n) PORT MAP(inp, out);

21 END my\_arch;

22 -----

**Example: ALU Made of COMPONENTS**

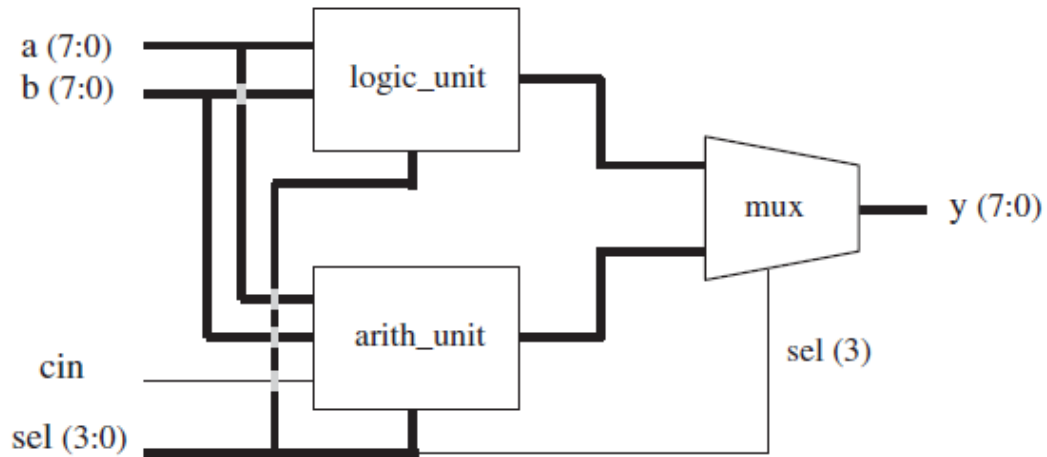

sel	Operation	Function	Unit
0000	y <= a	Transfer a	Arithmetic
0001	y <= a+1	Increment a	
0010	y <= a-1	Decrement a	
0011	y <= b	Transfer b	
0100	y <= b+1	Increment b	
0101	y <= b-1	Decrement b	
0110	y <= a+b	Add a and b	
0111	y <= a+b+cin	Add a and b with carry	
1000	y <= NOT a	Complement a	
1001	y <= NOT b	Complement b	
1010	y <= a AND b	AND	
1011	y <= a OR b	OR	
1100	y <= a NAND b	NAND	
1101	y <= a NOR b	NOR	
1110	y <= a XOR b	XOR	
1111	y <= a XNOR b	XNOR	

```

1 ----- COMPONENT arith_unit: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 USE ieee.std_logic_unsigned.all;
5 -----
6 ENTITY arith_unit IS
7     PORT ( a, b: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
8           sel: IN STD_LOGIC_VECTOR (2 DOWNT0 0);
9           cin: IN STD_LOGIC;
10          x: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
11 END arith_unit;
12 -----
13 ARCHITECTURE arith_unit OF arith_unit IS
14     SIGNAL arith, logic: STD_LOGIC_VECTOR (7 DOWNT0 0);
15 BEGIN
16     WITH sel SELECT
17         x <= a WHEN "000",
18         a+1 WHEN "001",
19         a-1 WHEN "010",
20         b WHEN "011",
21         b+1 WHEN "100",
22         b-1 WHEN "101",
23         a+b WHEN "110",
24         a+b+cin WHEN OTHERS;
25 END arith_unit;

```

26 -----

1 ----- COMPONENT logic\_unit: -----

2 LIBRARY ieee;

3 USE ieee.std\_logic\_1164.all;

4 -----

5 ENTITY logic\_unit IS

6     PORT ( a, b: IN STD\_LOGIC\_VECTOR (7 DOWNT0 0);

7             sel: IN STD\_LOGIC\_VECTOR (2 DOWNT0 0);

8             x: OUT STD\_LOGIC\_VECTOR (7 DOWNT0 0));

9 END logic\_unit;

10 -----

11 ARCHITECTURE logic\_unit OF logic\_unit IS

12 BEGIN

13     WITH sel SELECT

14         x <= NOT a WHEN "000",

15             NOT b WHEN "001",

16             a AND b WHEN "010",

17             a OR b WHEN "011",

18             a NAND b WHEN "100",

19             a NOR b WHEN "101",

20             a XOR b WHEN "110",

21     NOT (a XOR b) WHEN OTHERS;

22 END logic\_unit;

23 -----

```

1 ----- COMPONENT mux: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY mux IS
6 PORT ( a, b: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
7       sel: IN STD_LOGIC;
8       x: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
9 END mux;
10 -----
11 ARCHITECTURE mux OF mux IS
12 BEGIN
13   WITH sel SELECT
14     x <= a WHEN '0',
15     b WHEN OTHERS;
16 END mux;
17 -----

```

```

1 ----- Project ALU (main code): -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY alu IS
6   PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNT0 0);

```

```

7         cin: IN STD_LOGIC;
8         sel: IN STD_LOGIC_VECTOR(3 DOWNTO 0);
9         y: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
10 END alu;
11 -----
12 ARCHITECTURE alu OF alu IS
13 -----
14 COMPONENT arith_unit IS
15     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
16           cin: IN STD_LOGIC;
17           sel: IN STD_LOGIC_VECTOR(2 DOWNTO 0);
18           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
19 END COMPONENT;
20 -----
21 COMPONENT logic_unit IS
22     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
23           sel: IN STD_LOGIC_VECTOR(2 DOWNTO 0);
24           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
25 END COMPONENT;
26 -----
27 COMPONENT mux IS
28     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
29           sel: IN STD_LOGIC;
30           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
31 END COMPONENT;

```

```
32 -----
33 SIGNAL x1, x2: STD_LOGIC_VECTOR(7 DOWNTO 0);
34 -----
35 BEGIN
36   U1: arith_unit PORT MAP (a, b, cin, sel(2 DOWNTO 0), x1);
37   U2: logic_unit PORT MAP (a, b, sel(2 DOWNTO 0), x2);
38   U3: mux PORT MAP (x1, x2, sel(3), y);
39 END alu;
40 -----
```