

ECE 476 MICROCOMPUTER ENGINEERING

FINAL EXAM, JUNE 10, 2009.

Open book. Duration 2.5 hours. There are 6 questions.

Write your name on every page. Use the back of the pages for answers. Explain yourself clearly and work diligently.

① Two VHDL codes are given as

a)

```
SIGNAL Z, A, B, C, D: std_logic;  
BEGIN  
  Z <= A AND B;  
  Z <= C AND D;
```

b)

```
SIGNAL Z, A, B, C, D: std_logic;  
BEGIN  
  PROCESS (A, B, C, D)  
    BEGIN  
      Z <= A AND B;  
      Z <= C AND D;  
    END PROCESS;
```

Draw the corresponding logic circuits to these VHDL codes.


② a) Design a counter with T flip-flops and combinational circuit such that when $\text{Resetn} = 0$, it should asynchronously returns to "00" state; when $\text{Resetn} = 1$ it should count the sequence 00, 10, 01, 11, 00 ... when $w = 1$, and count the same sequence backwards (i.e., 00, 11, 01, 10, 00, 11 ...) when $w = 0$.

b) Write the VHDL code for this finite state machine (FSM).

③ Develop and write the VHDL code for the FSM that detects the sequences 101 and 010 on the signal w . An example of the sequence and the output z is given as:

w : 00001011010110001010100000
 z : 00000001100111000000111000

 ④ Write the VHDL code to implement the circuit




⑤ You want to monitor available spaces in a 100-space parking garage and you need to

- provide an indication of a FULL condition when there is no empty space by illuminating a display sign, and

- lowering a gate bar at the entrance when there are empty spaces available for an incoming car.

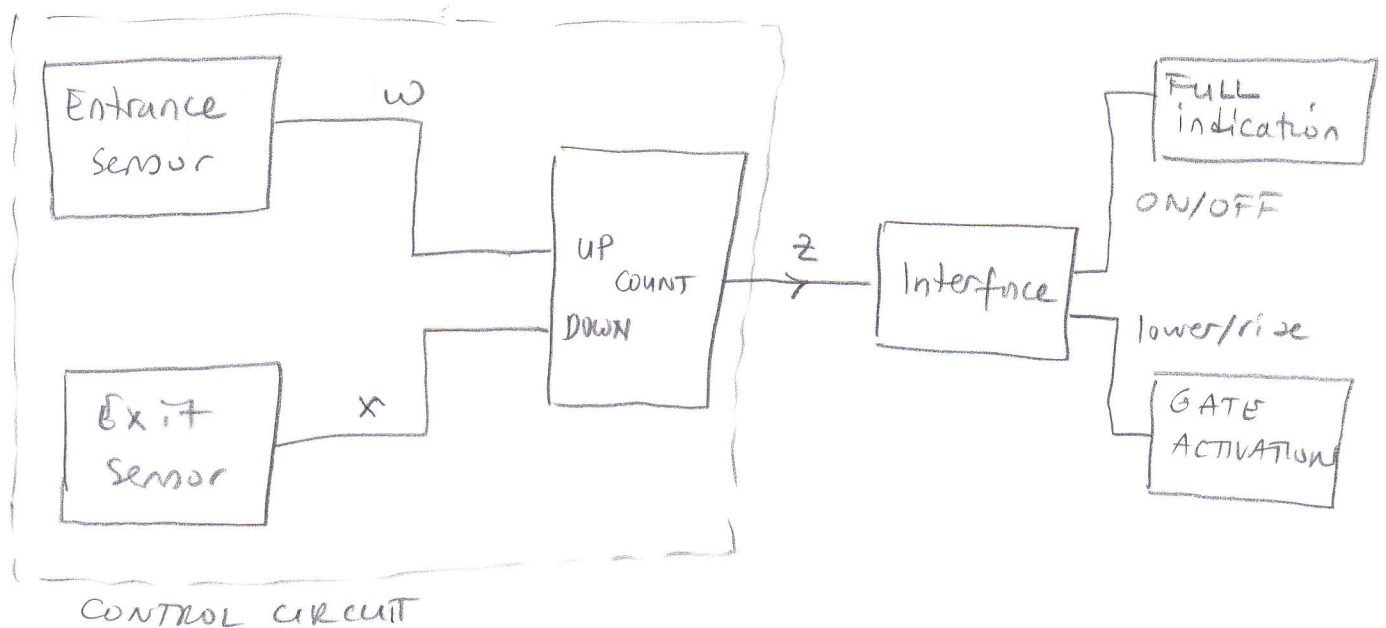Functional block diagram of the monitoring circuit would be:



Assuming an entrance and exit do not occur at the same time,

a) Design the control circuit

b) Write the VHDL code for the control circuit

NOTE: Inputs are w , x , clock, Reset
 output is z (when $z=1$ garage is Full, when $z=0$ the garage is empty (there are available spaces) and the gate bar can be lowered when there is an incoming car to park.)

⑥ Two VHDL codes are given as

```
ENTITY CIRCUIT IS  
  PORT ( D, CLK : IN STD-LOGIC;  
         Q : OUT STD-LOGIC);  
END CIRCUIT
```

a) ARCHITECTURE BEHAVIOR OF CIRCUIT IS

```
BEGIN  
  PROCESS (D, CLK)  
  BEGIN  
    IF CLK = '1' THEN  
      Q1 <= D;  
    END IF;  
  END PROCESS;  
END BEHAVIOR;
```

b) ARCHITECTURE BEHAVIOR OF CIRCUIT IS

```
BEGIN  
  PROCESS  
  BEGIN  
    WAIT UNTIL CLK'EVENT AND CLK = '0';  
    Q2 <= D;  
  END PROCESS;  
END BEHAVIOR;
```

If we simulate and test the VHDL codes above, with the signals given below, draw Q1 and Q2

