

ECE 476 MID-TERM EXAM

APRIL 22th, 2010-04-20

4 questions. Total 100 points. Exam duration 2 hours. Open book, open notebook. No use of laptops, mobile phone or any wireless device. Print your name on every page.

1. Two VHDL codes are given as (10p)


```
a. SIGNAL Z, A, B, C, D: STD_LOGIC;  
BEGIN  
Z<=A AND B;  
Z<=C OR D;  
END BEHAVIOR;
```

```
b. SIGNAL Z, A, B, C, D: STD_LOGIC;  
BEGIN  
PROCESS(A, B, C, D)  
BEGIN  
Z<=A AND B;  
Z<=C OR D;  
END PROCESS;  
END BEHAVIOR;
```

Show the corresponding logic circuits to these VHDL codes.


2. To prevent the ripple in the adders, a design can be made and used as shown below. The circuit immediately calculates the carry bit generated in a full adder. (40p)

 - a. Explain how this circuit calculates the carry bit.
- b. Write all the the required VHDL codes to implement this circuit (A1, B1, C0 inputs, C1 output, all one-bit) by using the 2-to-1 mux as a component, using a concurrent conditional statement.
- c. Write all the required VHDL codes to implement this circuit by using the 2-to-1 mux as a package, using a concurrent SELECT statement.



Student Number and Name :

 3. Provide the structural VHDL code for the circuit given below. (Use a 1-bit Full Adder (FA) as a package, and for-GENERATE statement in your code). (25p)



4. Consider an FPGA-operated heater shown below. This circuit is required to enable the ON/OFF control of the heater to adjust the temperature to a predefined temperature T_d . The desired control is such that the desired (T_d) and the measured (T_m) temperatures are converted into unsigned digital data of 4-bit and fed into the FPGA module. The FPGA outputs a control signal Y to control the heater such that the heater is turned on ($Y=1$) when the measured temperature is lower than the desired, and turned off ($Y=0$) otherwise. Provide the VHDL code of the circuit (use PROCESS statement in the coding). (25p)

